

# Two Bit Phase Shifter

JHU MMIC Project


EE525.787 FALL 2006

David J. Wendland



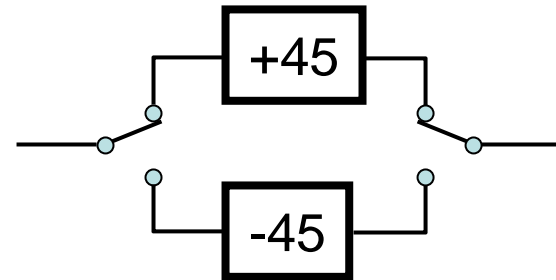
# Design Philosophy


- The topology of the design was set such that there was a relative phase shift through the network when compared to the zero or through path. The phase shifter consists of three sections.
  - Control
  - 90 degree shift
  - 180 degree shift
- The control section consists of circuitry to convert positive 5 volt control voltage to the appropriate voltages to the phase switches.
- The 90 and 180 degree shift sections are the same except for the amount of phase shift provided by each section.
- Each phase shift section consists of a positive phase network and a negative phase network.
- The through path passes through the positive phase network of each section.
- Let's walk through the 90 degree phase section.
- The 90 degree phase shift section consists of a positive 45 deg. phase shift network and a negative 45 deg. phase shift network. If the through path is set through the positive phase shift network. There will be a 90 degree relative phase when the path switches, from the +45 degree network to the -45 degree network.
- With the above described topology, the phase of the through path is arbitrary and is not important for the relative phase shift.
- The 180 degree phase shift is achieved the same way but using +/-90degree networks





## + 45 Degree Network

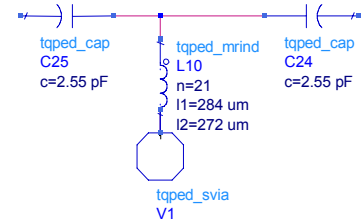


## -45 Degree Network

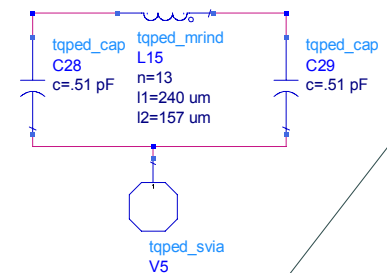

# Design Philosophy

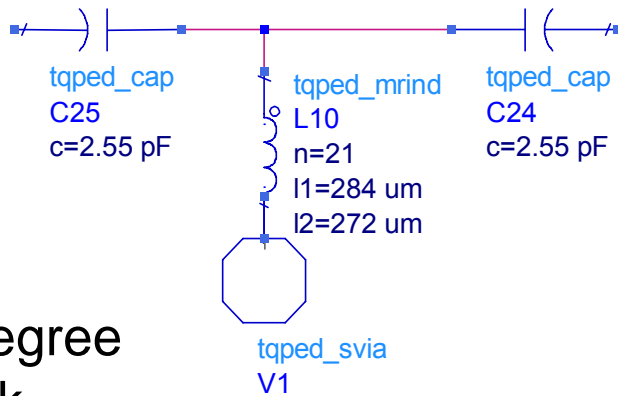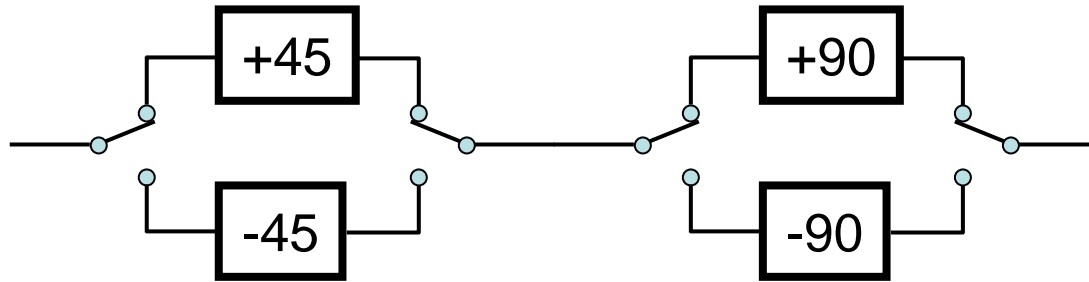


+ 45 Degree Network

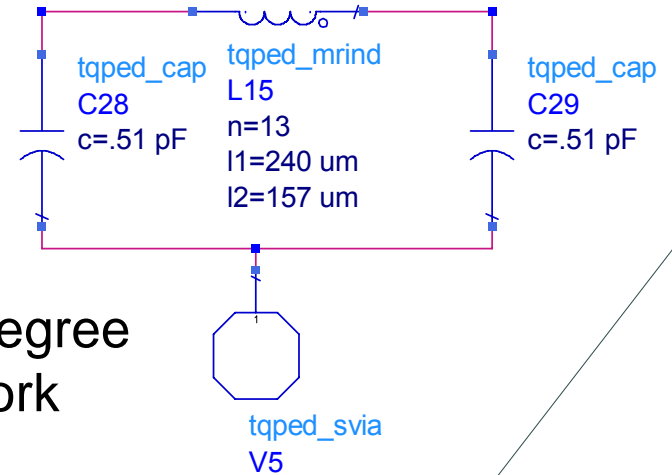

-45 Degree Network
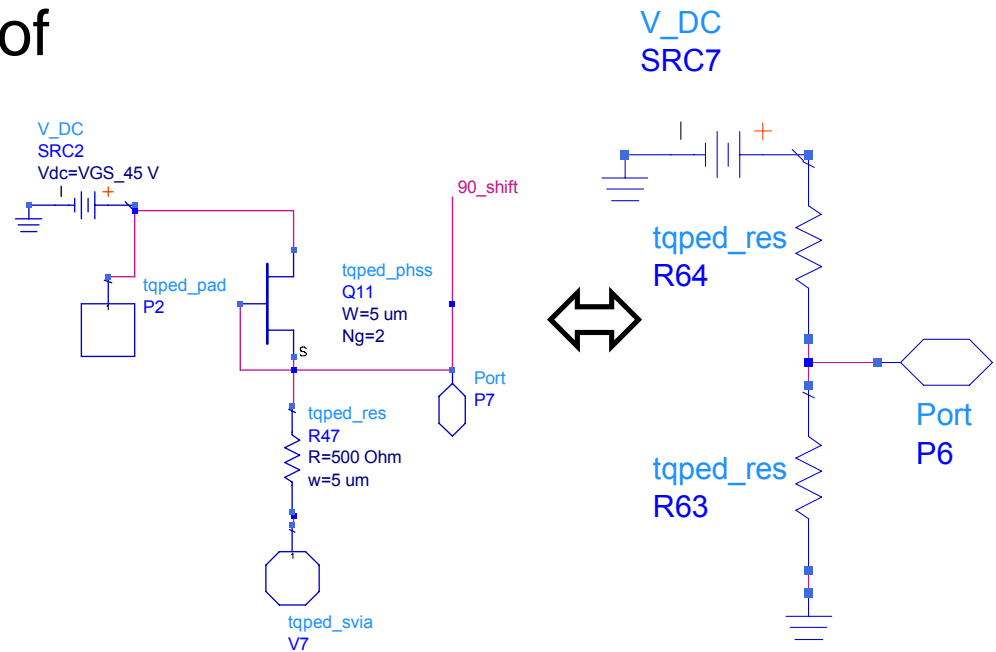
# Design Philosophy

- Emode transistor were used to take advantage of the positive gate bias
  - Can use single positive supply
- Dmode transistor were used to convert +5V to the desired gate voltage
  - Smaller than resistors
  - Save space in voltage dividers.
  - FET sized to provide:
    - 2mA for 45/90 bit
    - 4mA for +5V bias



Dmode FET in voltage divider


# Logic Table

Phase Shift	Bit 45	Bit 90
0	0	0
90	5	0
180	0	5
270	5	5

# Simulation/Layout

- The phase shifter was first developed with ideal components
- TriQuint components were then substituted and retuned
- The components were then inserted into the layout, positioned and interconnects added
- The interconnects of the critical paths were simulated using microstrip elements in the schematic.
- Critical interconnects consist of:
  - Connections between switches, capacitors and inductors of the phase shift elements.
- Interconnect between the 90 degree phase shift section, 180 degree section and pads were not simulated since those paths do not affect the relative phase shift.

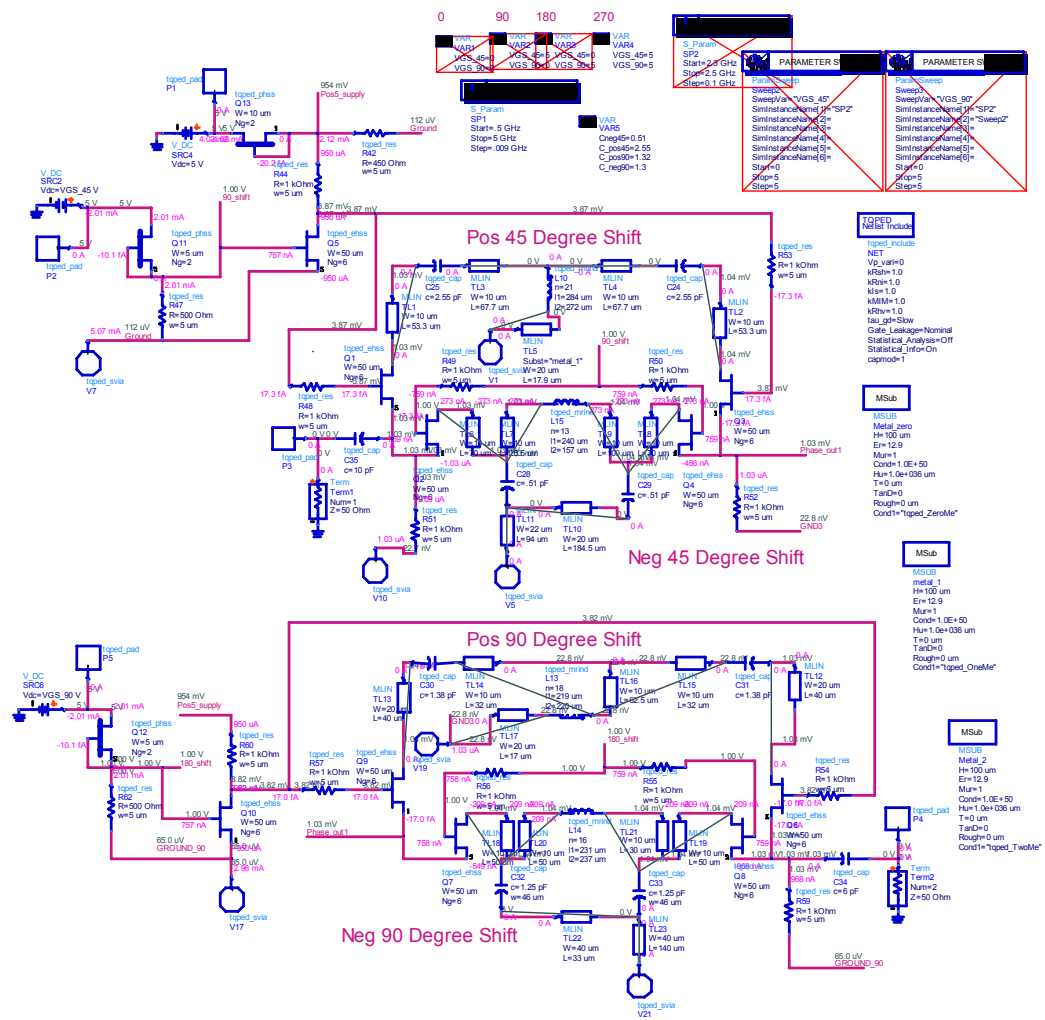
# Two Bit Phase Shifter Schematic with Interconnects









# 180 Degree Phase Shift


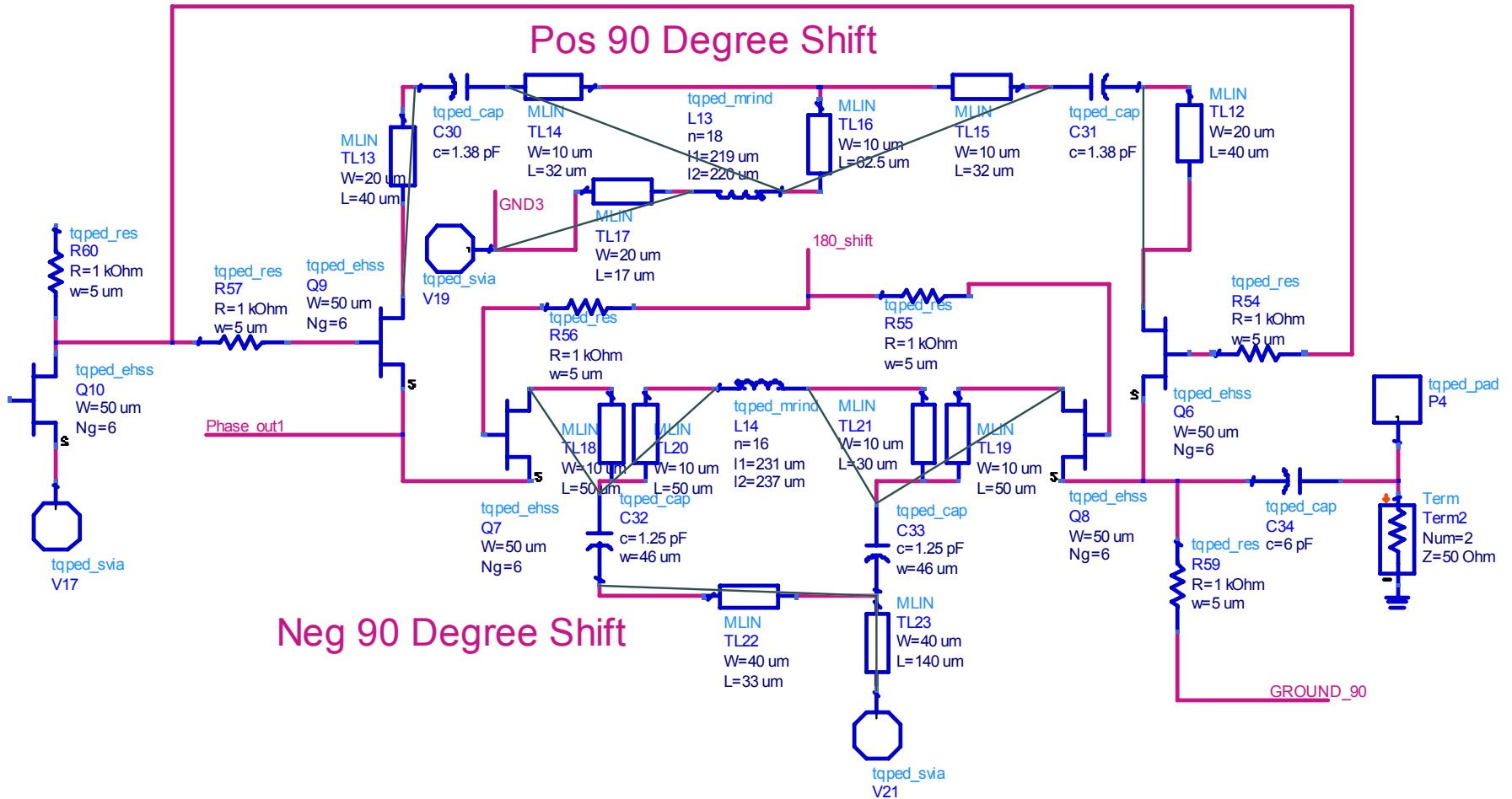


# DC Switch Bias Zero Degrees/Ref

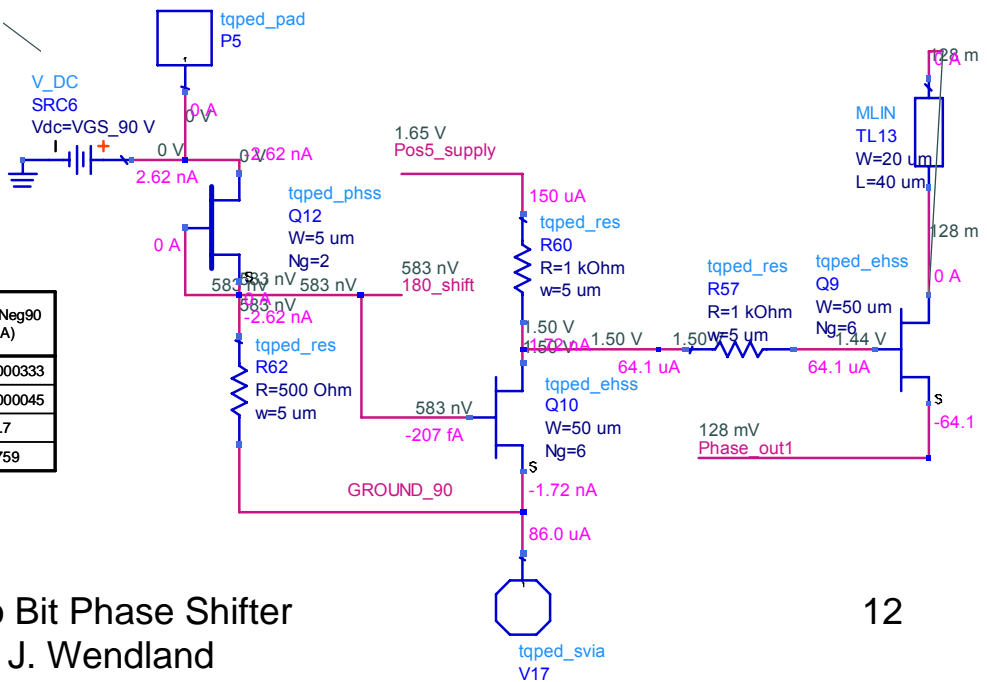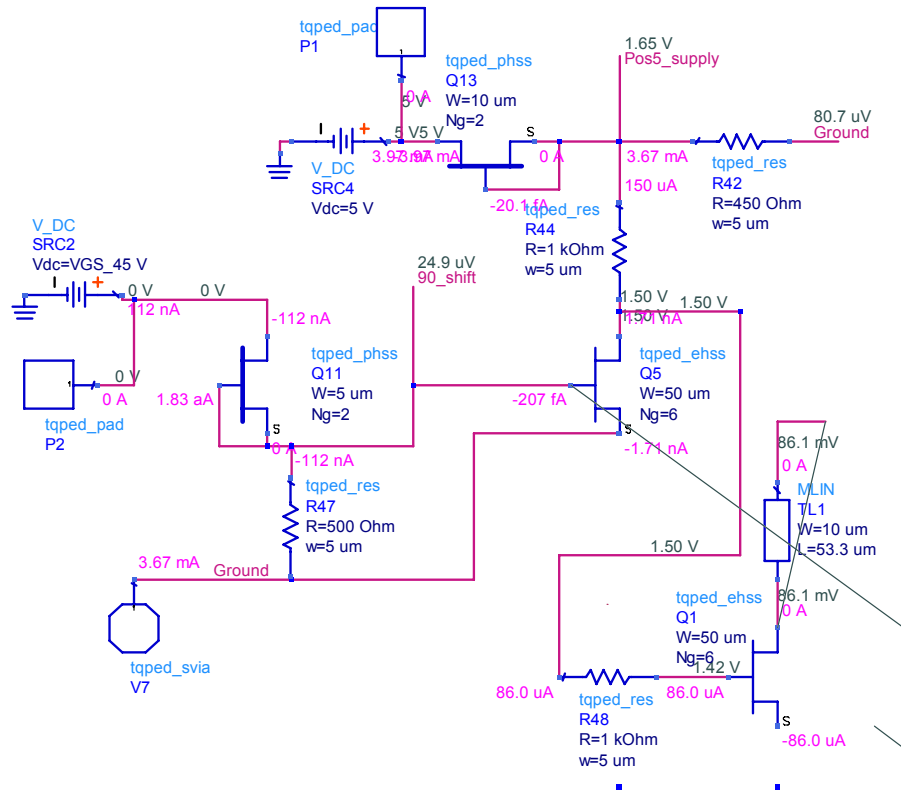



Phase Shift	Bit 45	Bit 90	Vgate Pos45 (V)	Vgate Neg45 (V)	Vgate Pos90 (V)	Vgate Neg90 (V)	Igate Pos45 (uA)	Igate Neg45 (uA)	Igate Pos90 (uA)	Igate Neg90 (uA)
0	0	0	1.42	2.50E-05	1.44	5.8E-07	86	0.000000306	64	0.000000333
90	5	0	0.005	1	1.2	7.8E-08	0.00000001	0.7	12	0.000000045
180	0	5	1.2	1.90E-05	0.005	1	0.000000045	0.000000011	0.7	
270	5	5	0.0039	1	3.82E-07	1	0.000000017	0.759	0.000000017	0.759

# DC Switch Bias 90 Degrees

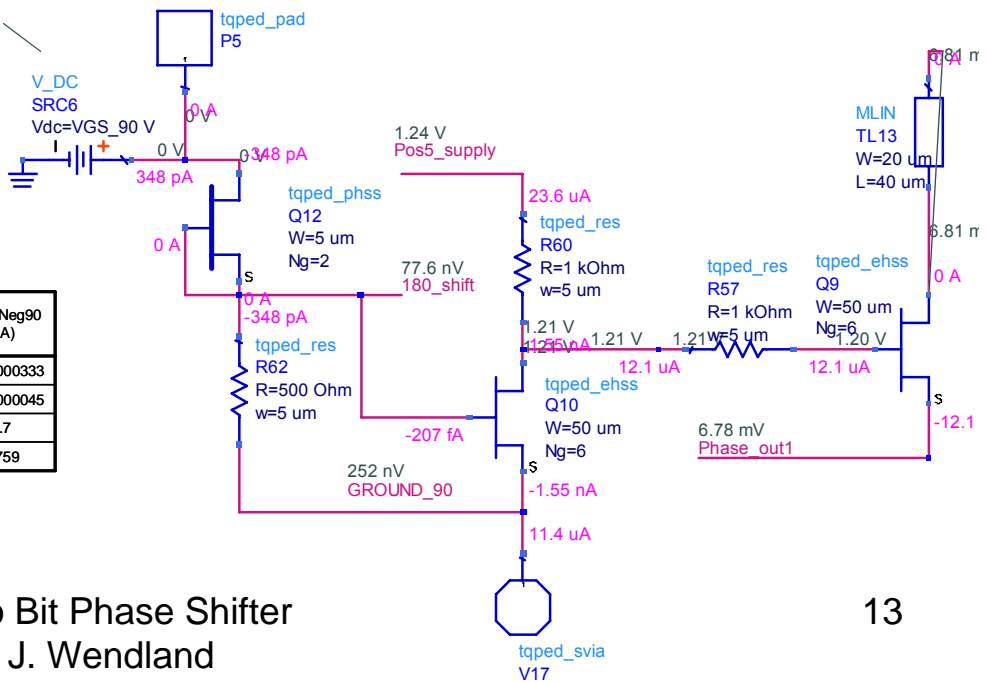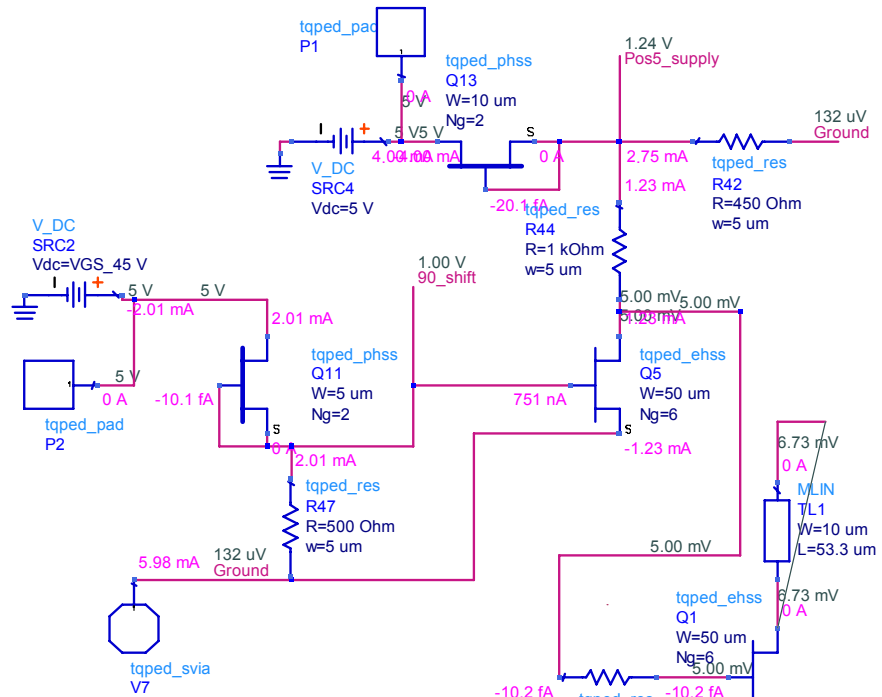



Phase Shift	Bit 45	Bit 90	Vgate Pos45 (V)	Vgate Neg45 (V)	Vgate Pos90 (V)	Vgate Neg90 (V)	Igate Pos45 (uA)	Igate Neg45 (uA)	Igate Pos90 (uA)	Igate Neg90 (uA)
0	0	0	1.42	2.50E-05	1.44	5.8E-07	86	0.000000306	64	0.000000333
90	5	0	0.005	1	1.2	7.8E-08	0.00000001	0.7	12	0.000000045
180	0	5	1.2	1.90E-05	0.005	1	0.000000045	0.000000011	0.7	
270	5	5	0.0039	1	3.82E-07	1	0.000000017	0.759	0.000000017	0.759

# DC Switch Bias 180 Degrees

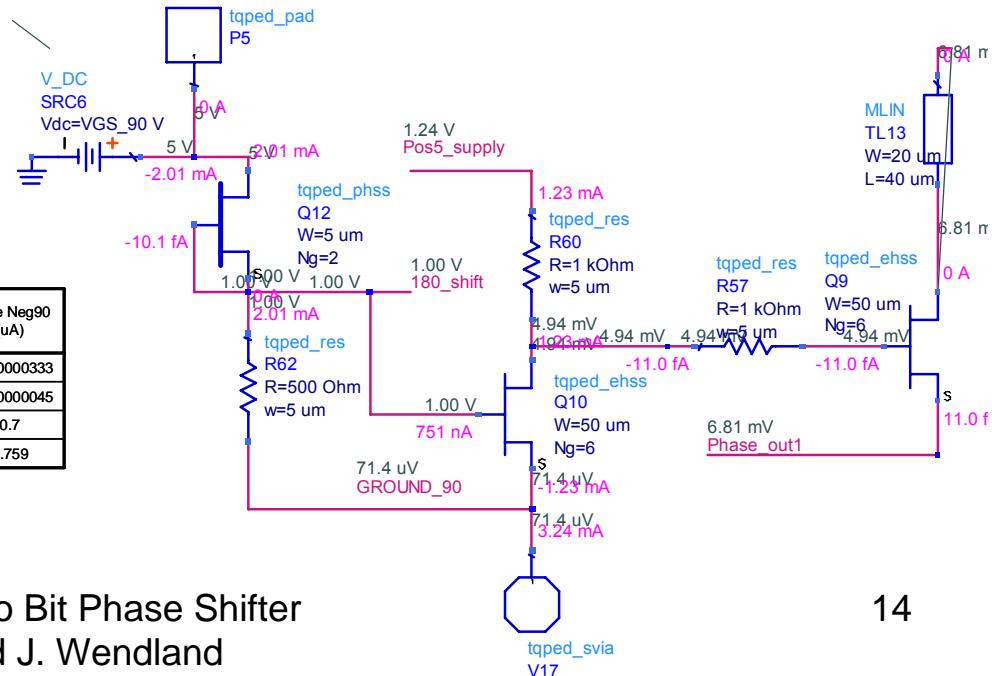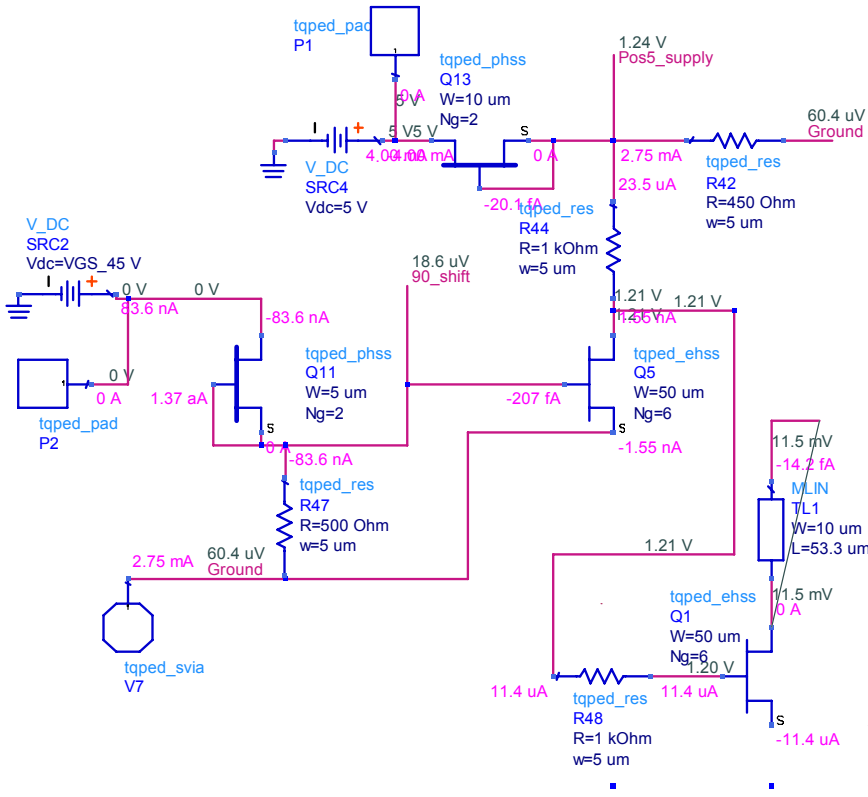

Phase Shift	Bit 45	Bit 90	Vgate Pos45 (V)	Vgate Neg45 (V)	Vgate Pos90 (V)	Vgate Neg90 (V)	Igate Pos45 (uA)	Igate Neg45 (uA)	Igate Pos90 (uA)	Igate Neg90 (uA)
0	0	0	1.42	2.50E-05	1.44	5.8E-07	86	0.000000306	64	0.000000333
90	5	0	0.005	1	1.2	7.8E-08	0.00000001	0.7	12	0.000000045
180	0	5	1.2	1.90E-05	0.005	1	0.000000045	0.000000011	0.7	
270	5	5	0.0039	1	3.82E-07	1	0.000000017	0.759	0.000000017	0.759

# DC Switch Bias 270 Degrees

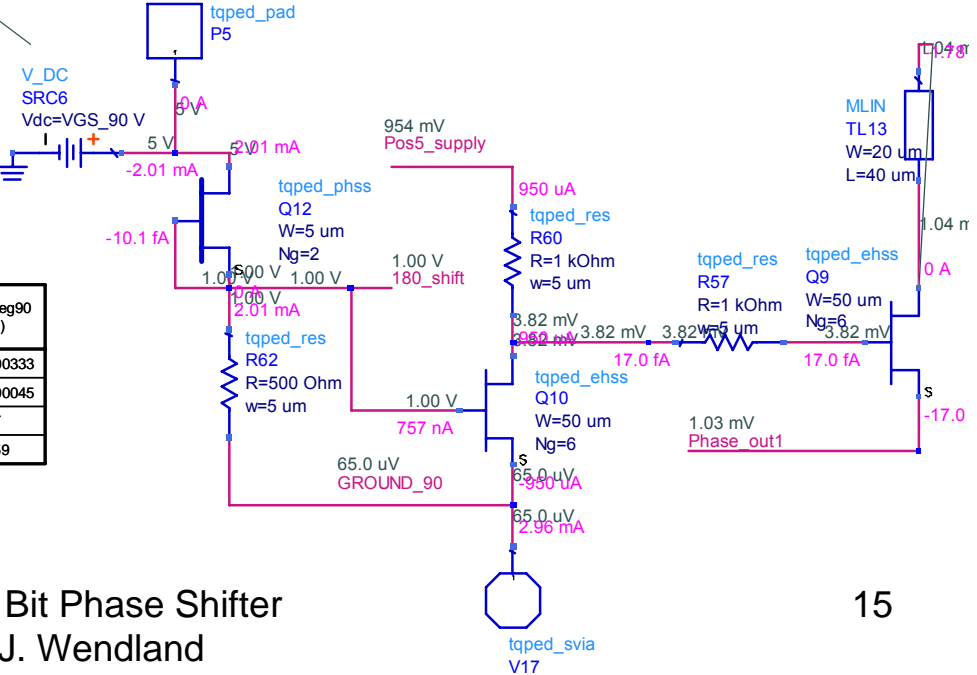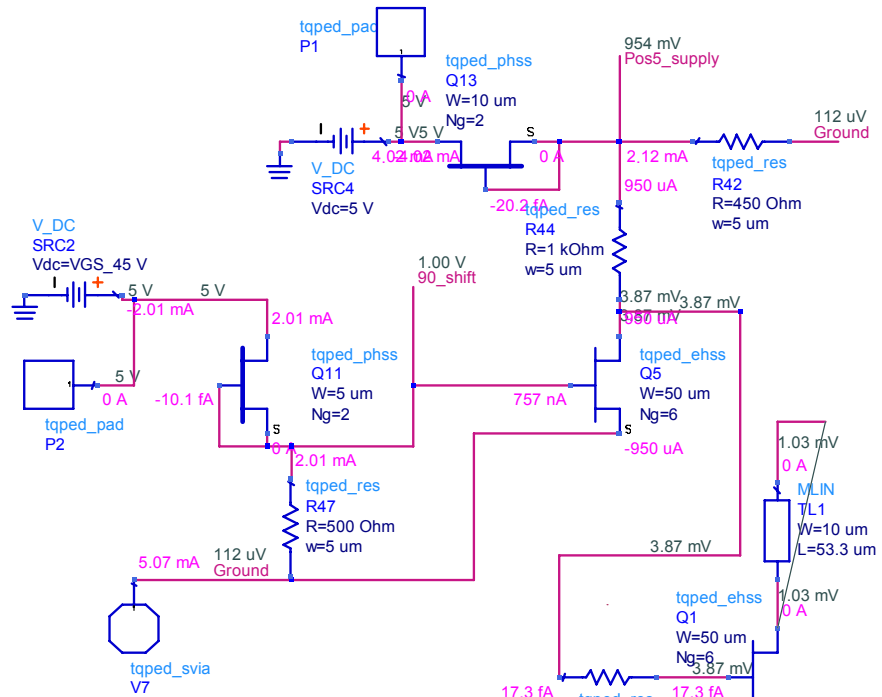

Phase Shift	Bit 45	Bit 90	Vgate Pos45 (V)	Vgate Neg45 (V)	Vgate Pos90 (V)	Vgate Neg90 (V)	Igate Pos45 (uA)	Igate Neg45 (uA)	Igate Pos90 (uA)	Igate Neg90 (uA)
0	0	0	1.42	2.50E-05	1.44	5.8E-07	86	0.000000306	64	0.000000333
90	5	0	0.005	1	1.2	7.8E-08	0.00000001	0.7	12	0.000000045
180	0	5	1.2	1.90E-05	0.005	1	11	0.000000045	0.000000011	0.7
270	5	5	0.0039	1	3.82E-07	1	0.000000017	0.759	0.000000017	0.759




# Design Specification

- Frequency: 2305 MHz to 2497 MHz
- Insertion loss: Less than 4dB (3dB Goal)
- Insertion Balance: +/- 1dB
- Phase shift: 90 and 180 degrees steps
- VSWR, 50 Ohms: Less than 1.5:1
- Supply Voltage: +/- 5 Volts
- Control Voltage: TTL(goal); or 0, -5V
- Size: 60x60 mil ANACHIP


# Achieved Specification

- The Specification of VSWR better than 1.5:1 was not achieved.
- A VSWR better than 1.8:1 was achieved
- Frequency(1.8:1 VSWR): 2300 MHz to 2642 MHz
- 1.8:1 VSWR Bandwidth: 342 MHz
- Insertion loss: 3.77 dB (2300 to 2500 MHz)  
3.96 dB (2300 to 2642 MHz)
- Insertion Balance: 0.45 dB (2300 to 2500 MHz)  
0.68 dB (2300 to 2642 MHz)


# Two Bit Phase Shifter Input VSWR

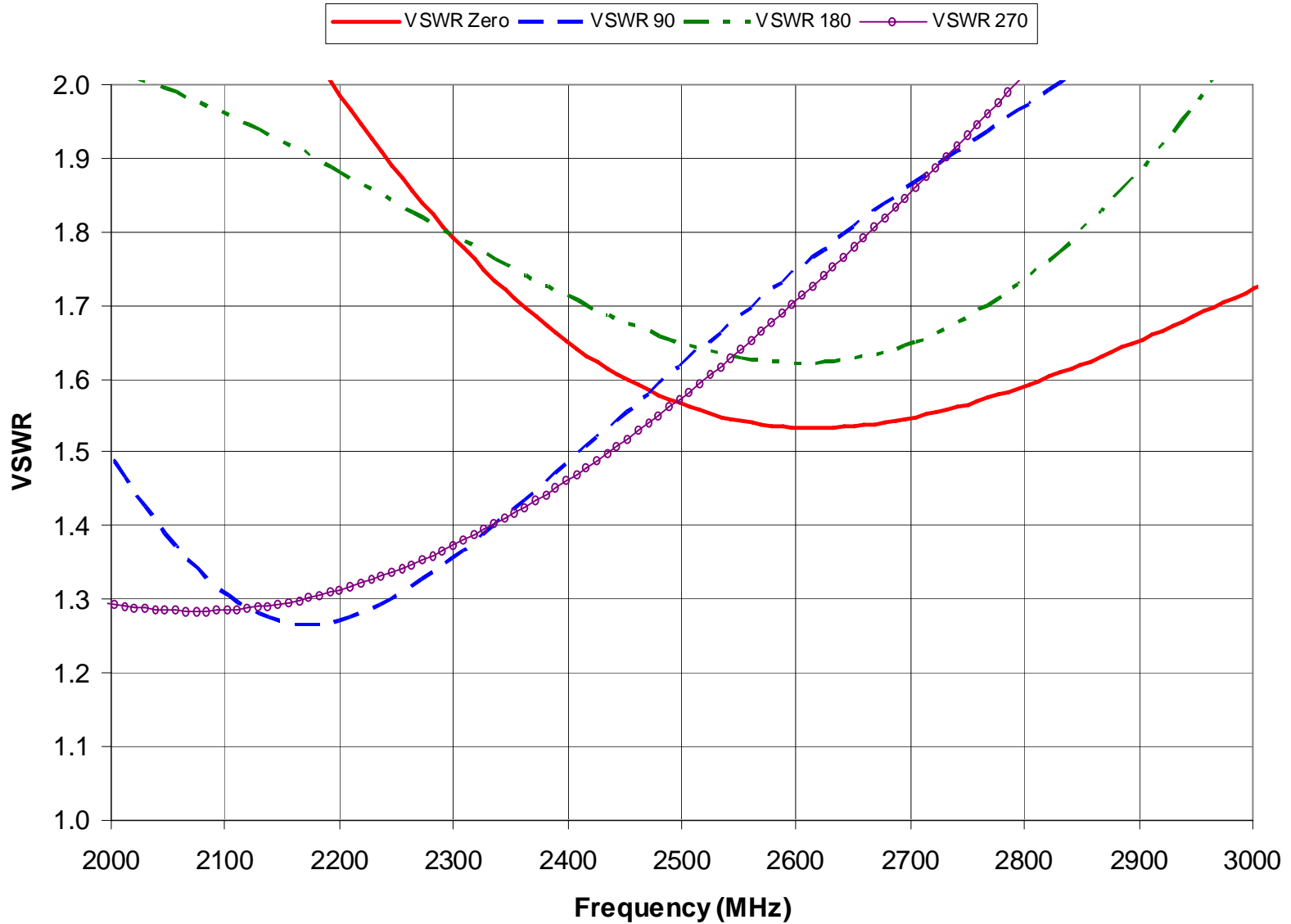

# Two Bit Phase Shifter Output VSWR

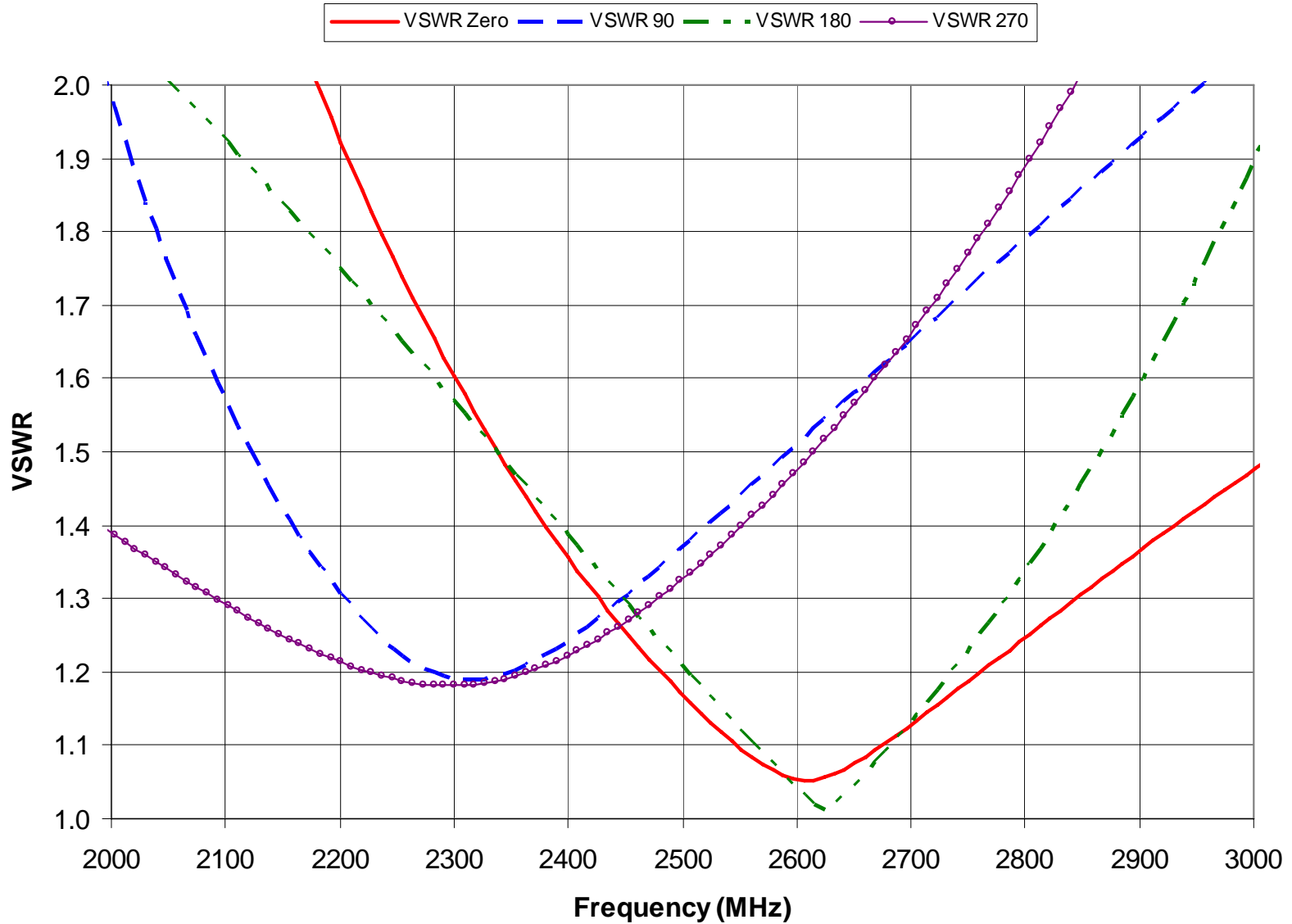

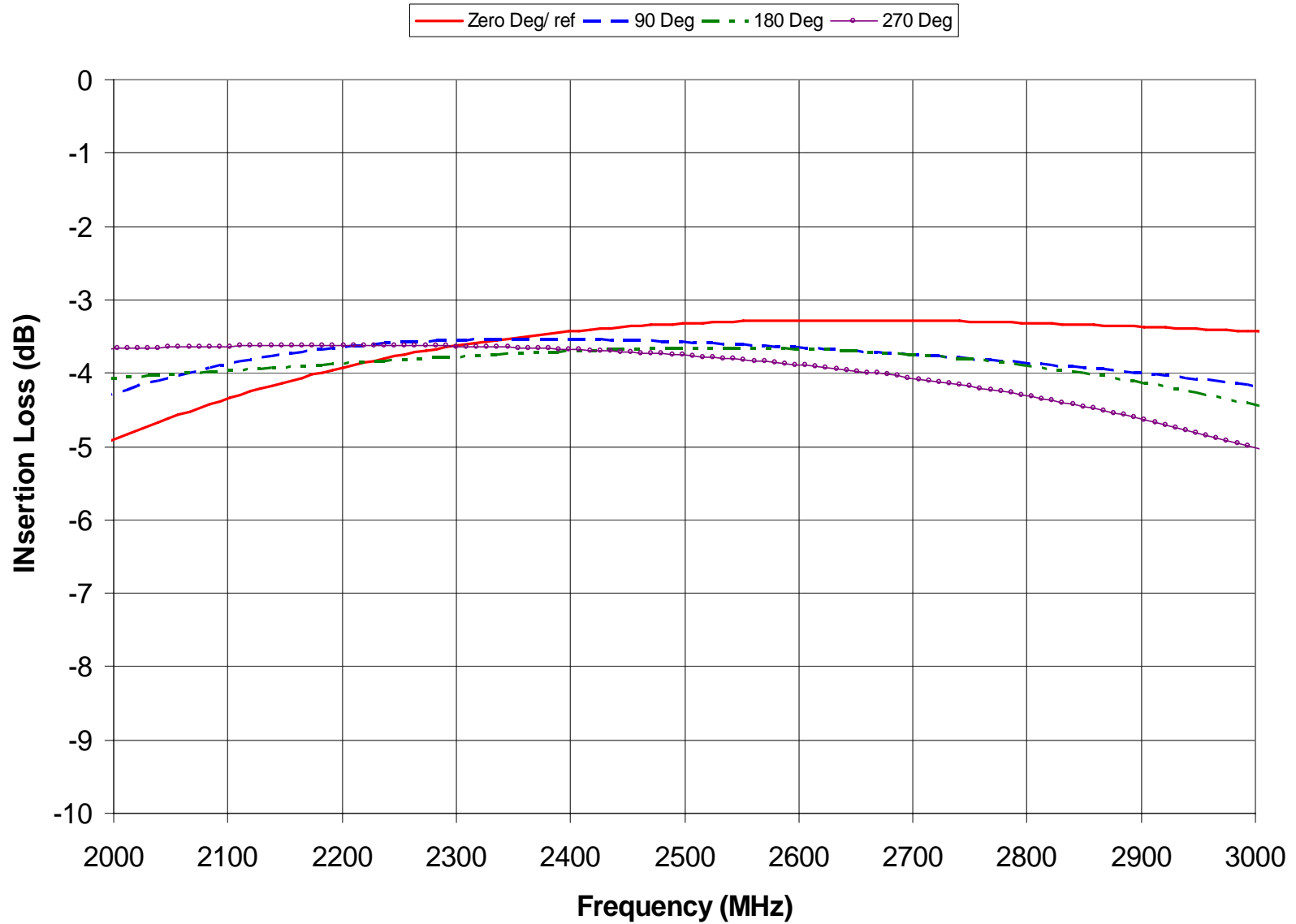
# Two Bit Phase Shifter Insertion Loss (S21)




# Achieved Specification

- Phase Shift: 90 and 180 degrees step
- Phase Flatness (2300 to 2500 MHz):
  - 90 Degree Shift -- 0.15 Deg.
  - 180 Degree Shift -- 1.4 Deg.
  - 270 Degree Shift -- 0.15 Deg.
- Phase Flatness (2300 to 2642 MHz):
  - 90 Degree Shift -- 0.53 Deg.
  - 180 Degree Shift -- 1.40 Deg.
  - 270 Degree Shift -- 0.49 Deg

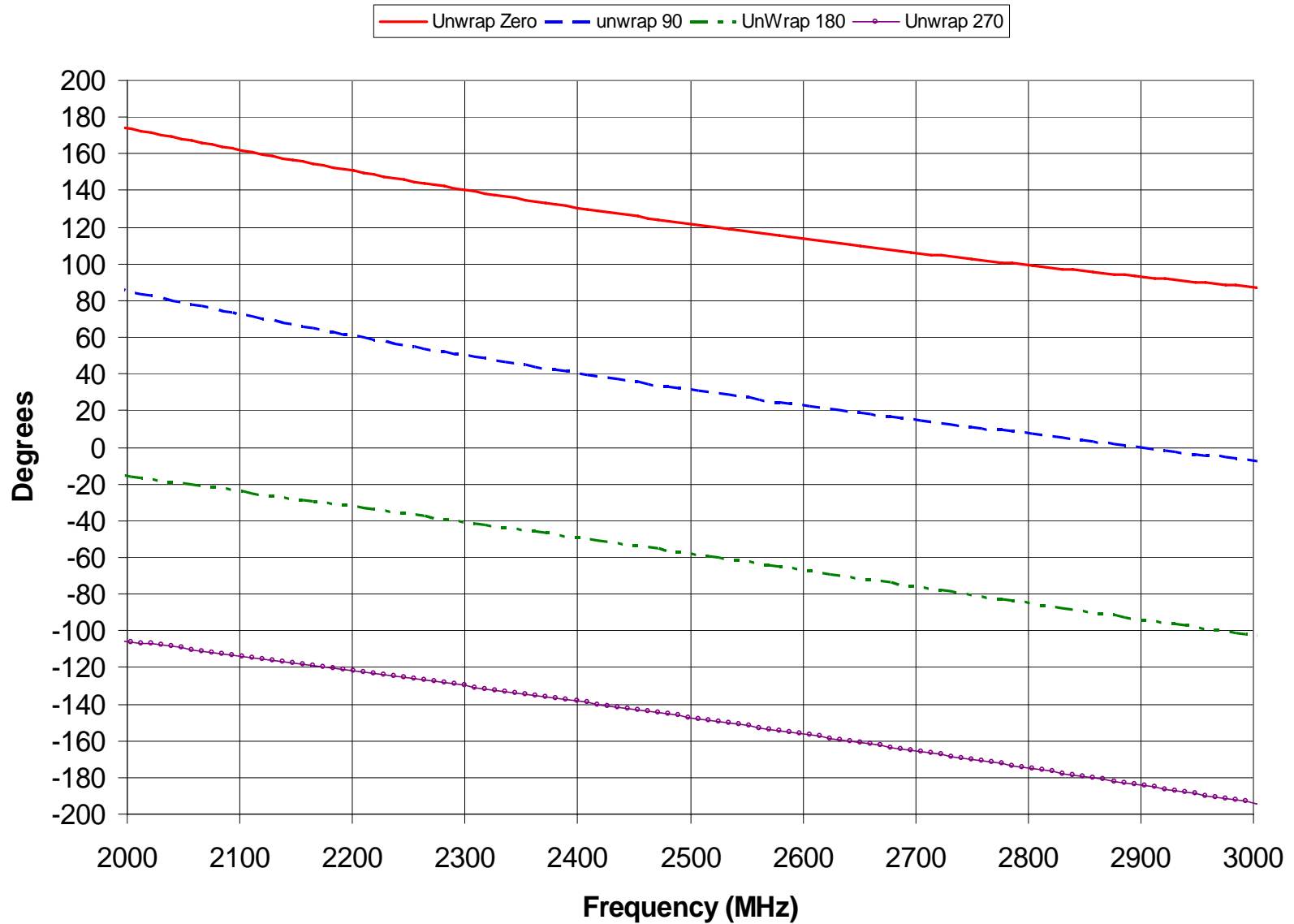
# Two Bit Phase Shifter Unwrap Phase (S21)



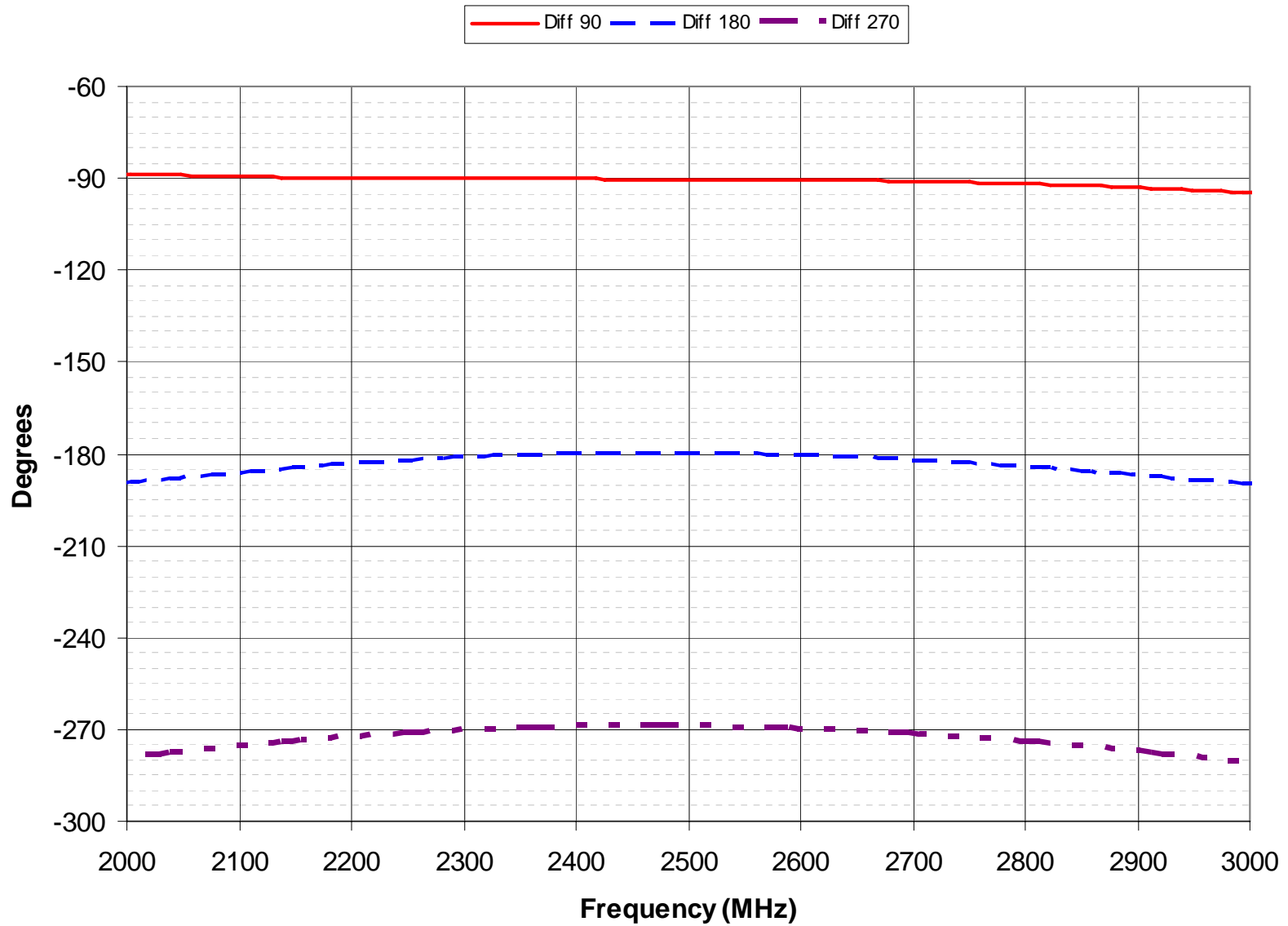
## Two Bit Phase Shifter; Phase Difference



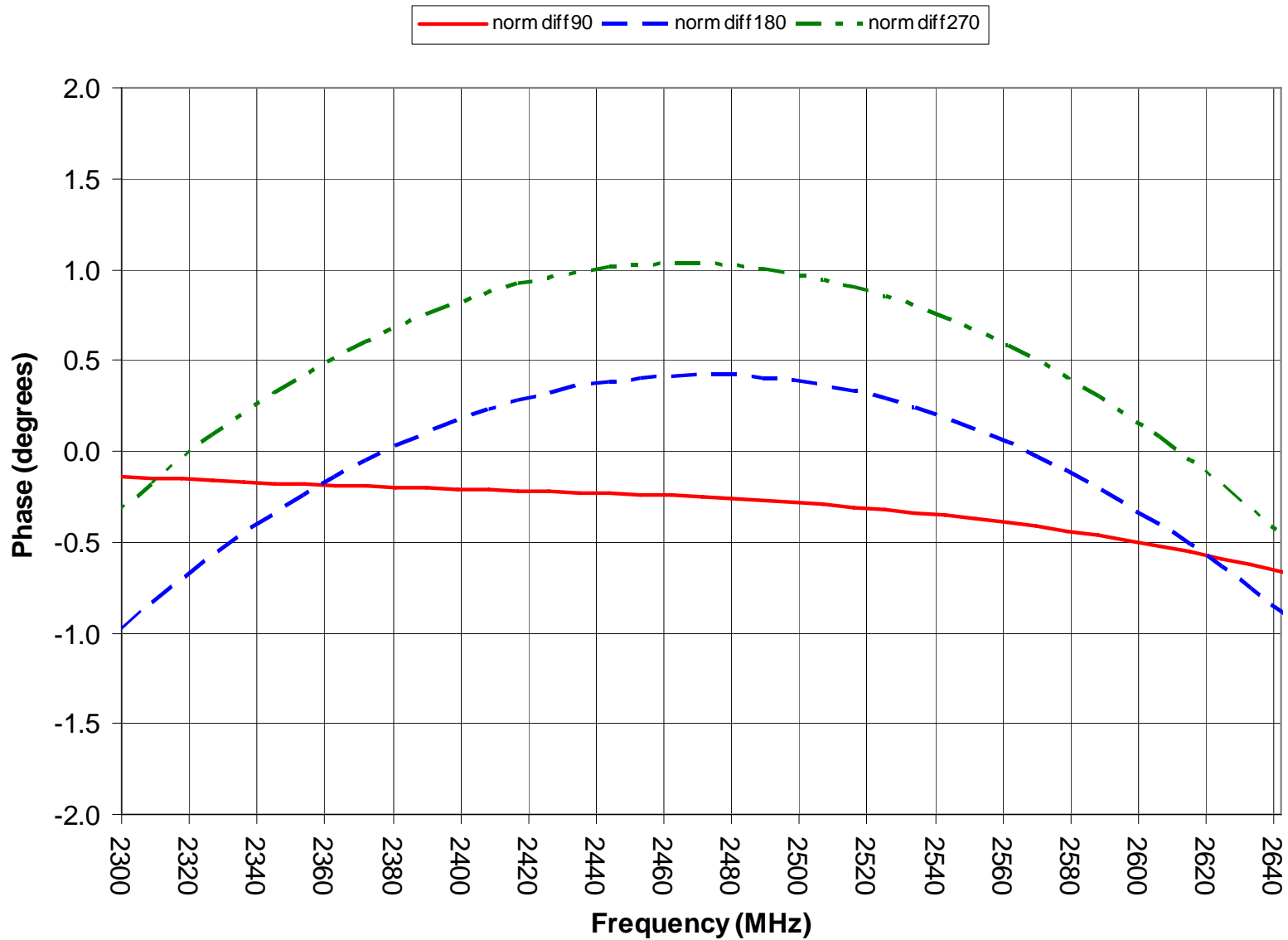
## Two Bit Phase Shifter: Normalized Phase Difference



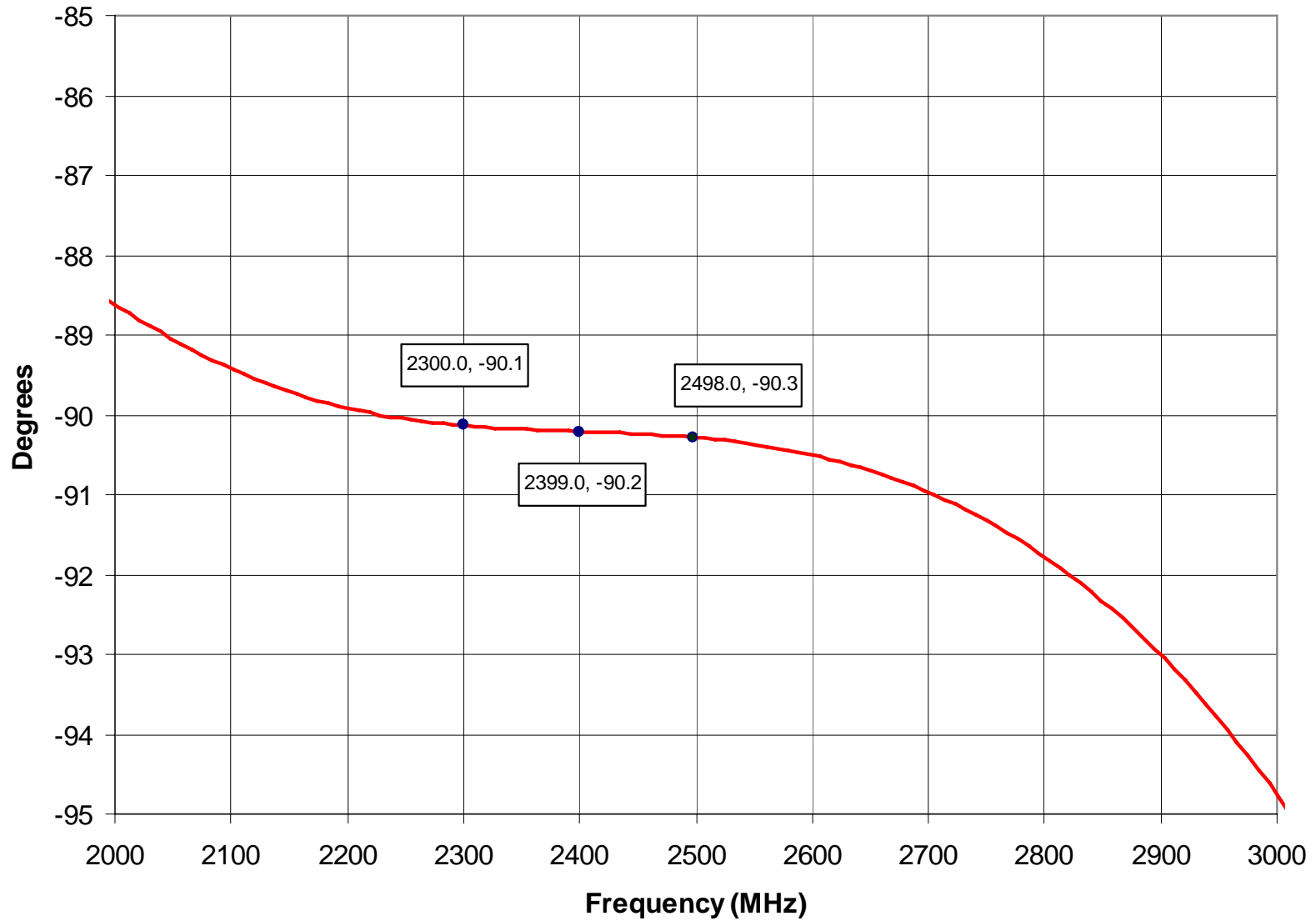
## Two Bit Phase Shifter; Phase Difference = 90 Degrees


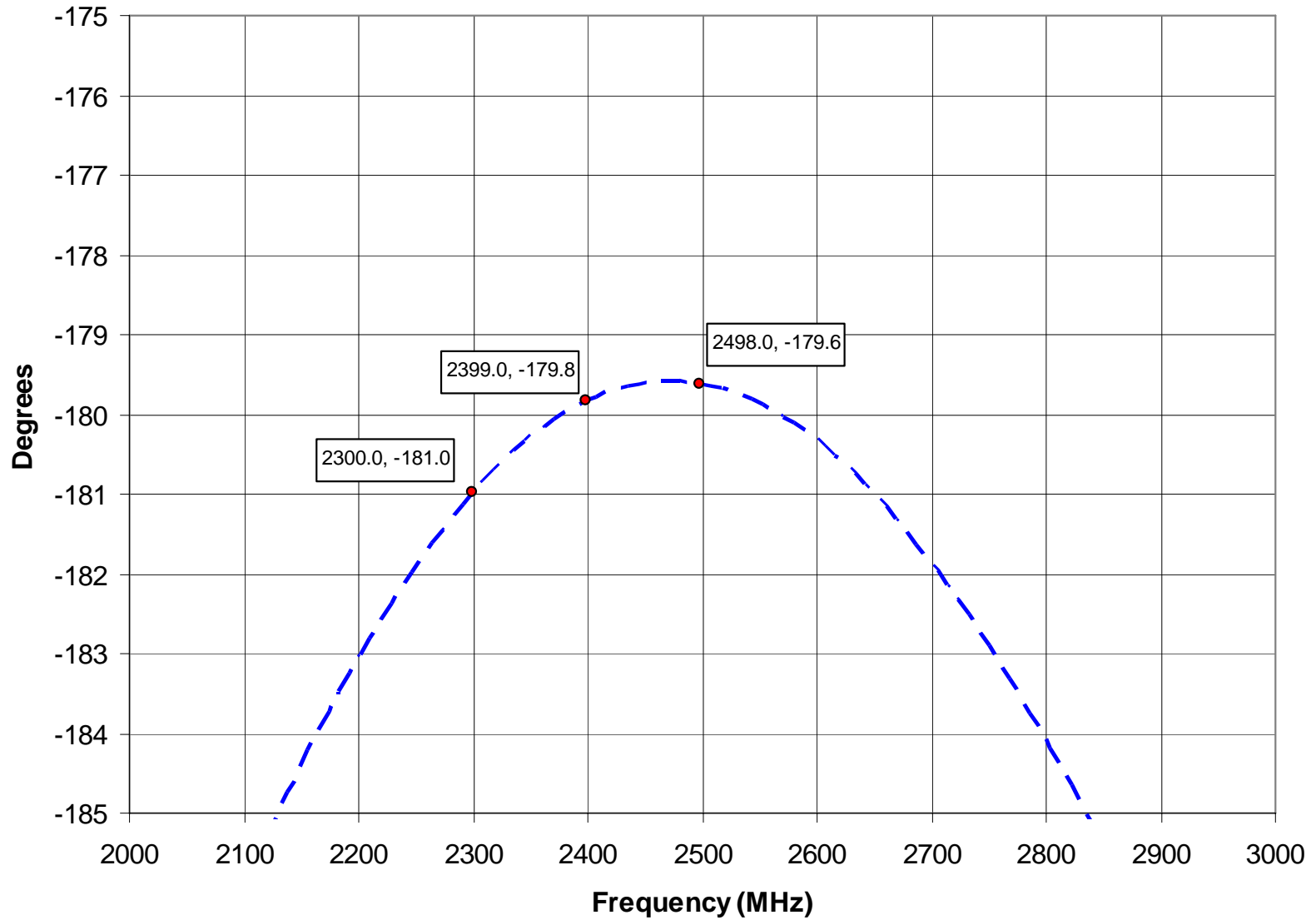
## Two Bit Phase Shifter; Phase Difference = 180 Degrees


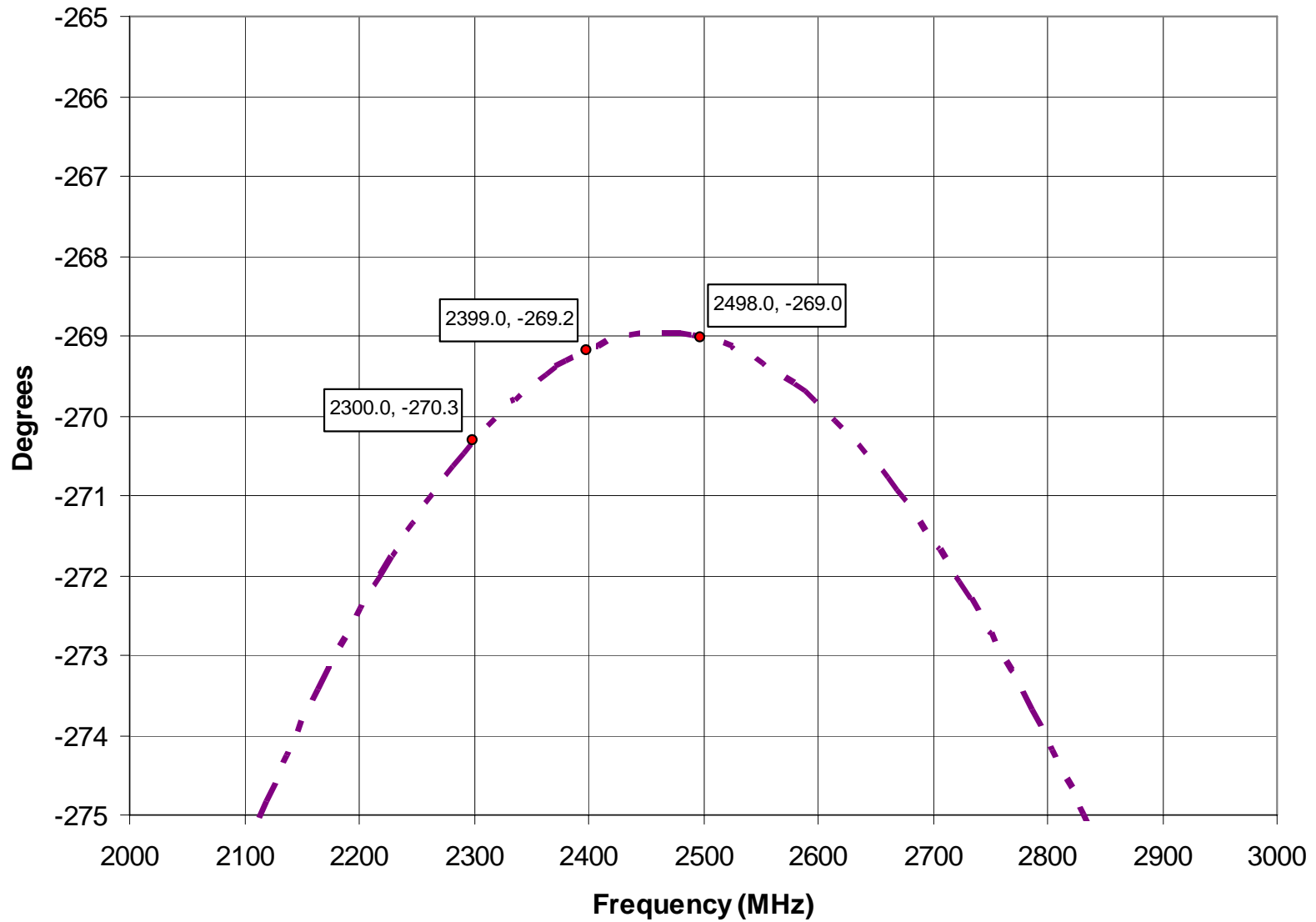
## Two Bit Phase Shifter; Phase Difference = 270 Degrees



# Achieved Specification

- Control Voltage is TTL (zero and +5V)
- Supply Voltage is +5 Volts
  
- Design fit on the 60 x 60 mil ANACHIP

# Things to look at


- Pay more attention to input VSWR
  - Concentrated on phase and insertion loss
- Switch size
  - Used default transistor size
  - A smaller switch may work as well while conserving space
- Wide Banding
  - Use two series 45 Deg element instead of a single 90 deg. element
- Switch gate voltage
  - Changed depending on phase selected

# DC Gate Bias


Phase Shift	Bit 45	Bit 90	Vgate Pos45 (V)	Vgate Neg45 (V)	Vgate Pos90 (V)	Vgate Neg90 (V)	Igate Pos45 (uA)	Igate Neg45 (uA)	Igate Pos90 (uA)	Igate Neg90 (uA)
0	0	0	1.42	2.50E-05	1.44	5.8E-07	86	0.000000306	64	0.000000333
90	5	0	0.005	1	1.2	7.8E-08	0.00000001	0.7	12	0.000000045
180	0	5	1.2	1.90E-05	0.005	1	11	0.000000045	0.000000011	0.7
270	5	5	0.0039	1	3.82E-07	1	0.000000017	0.759	0.000000017	0.759

# Backup Slides

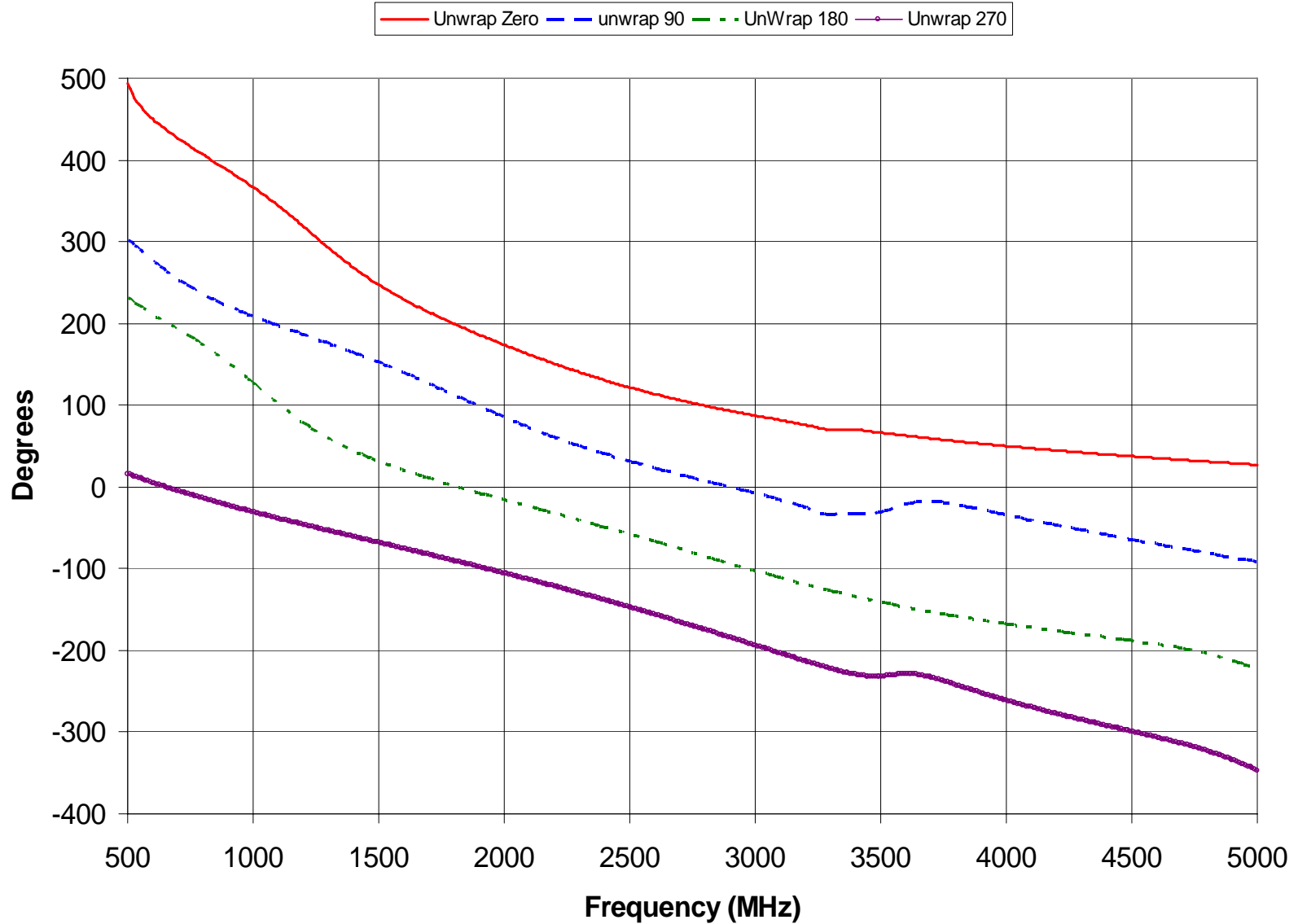
## Two Bit Phase Shifter Unwrap Phase (S21)



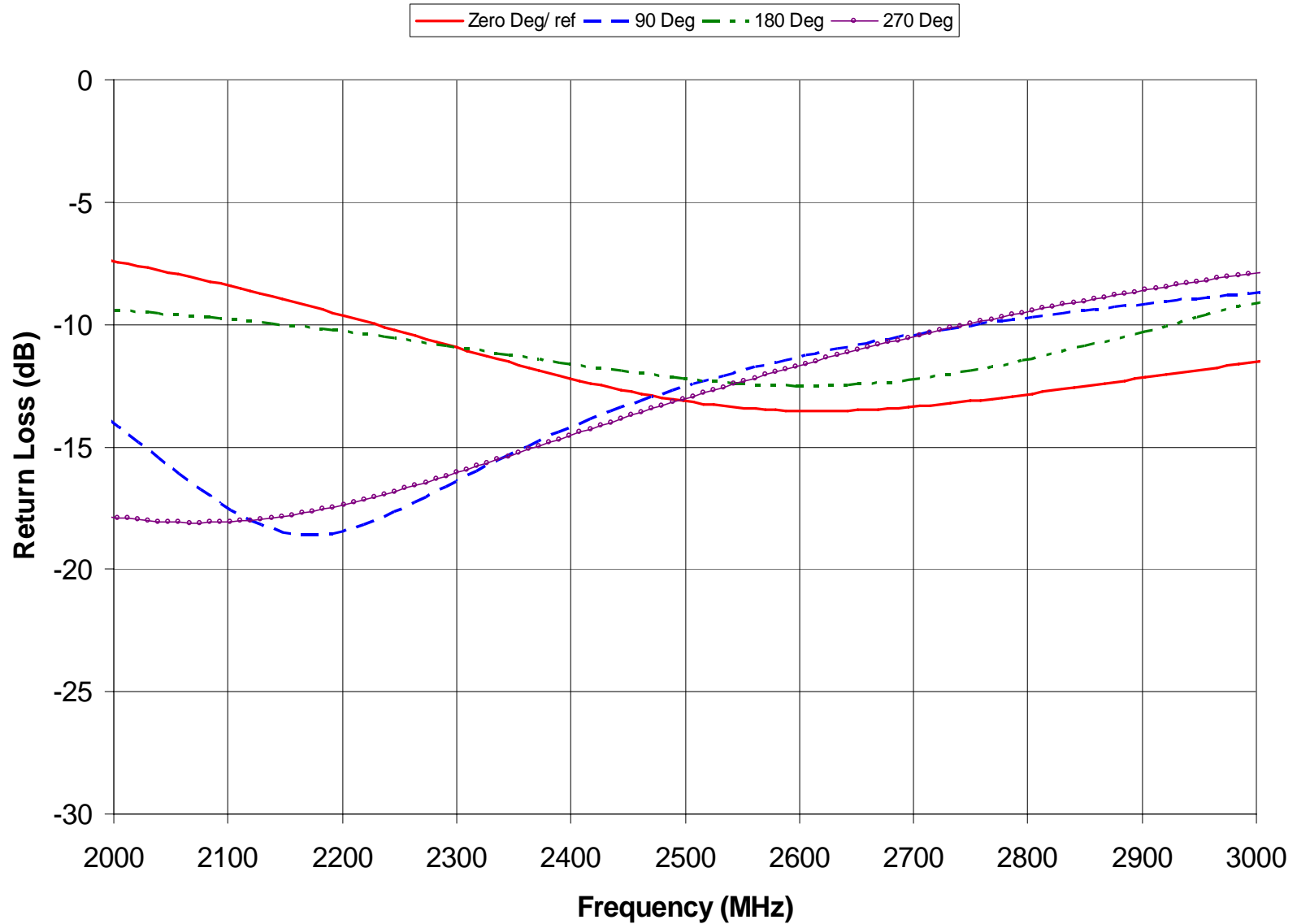
# Two Bit Phase Shifter Input Return Loss (S11)


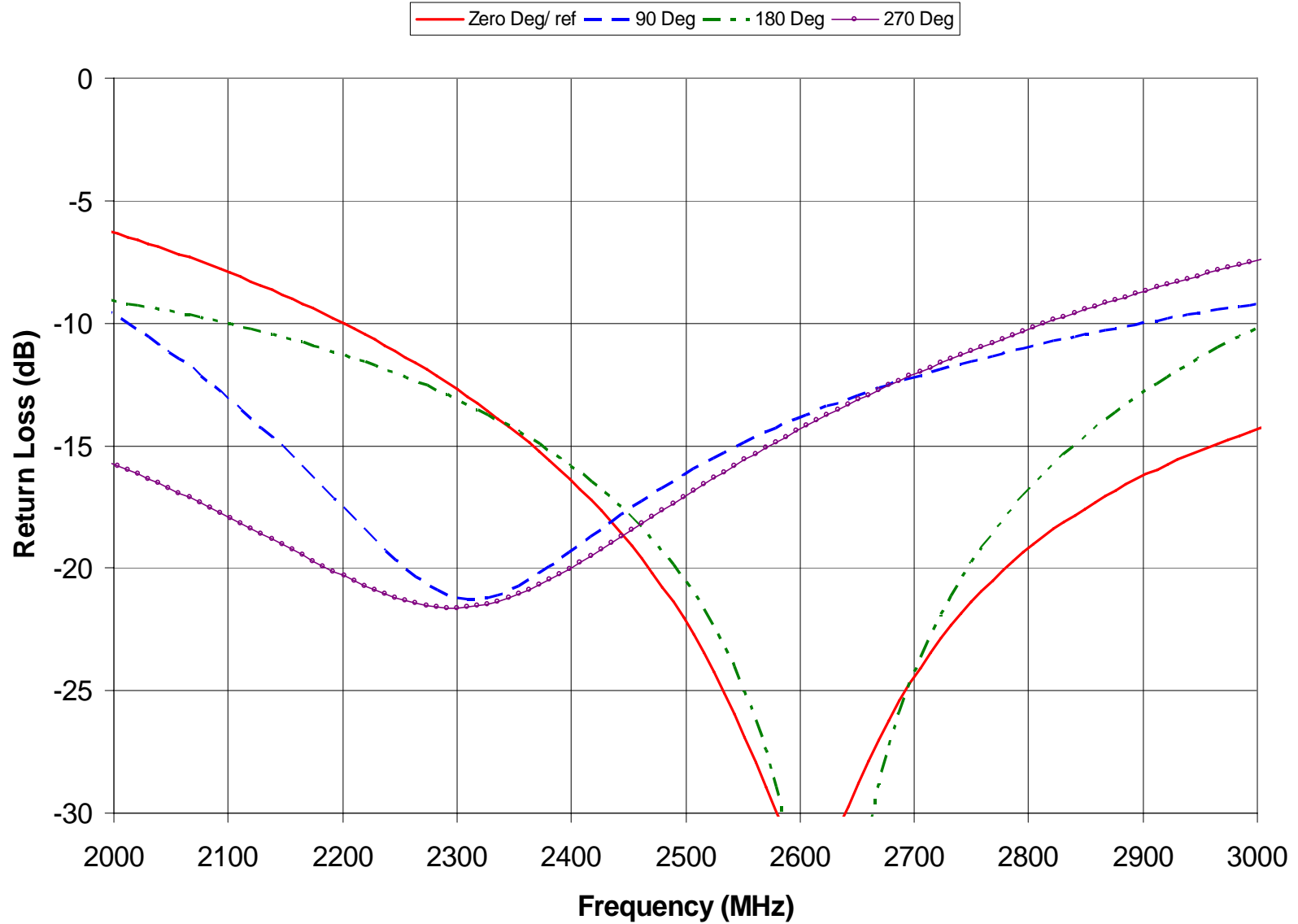
# Two Bit Phase Shifter Output Return Loss (S22)


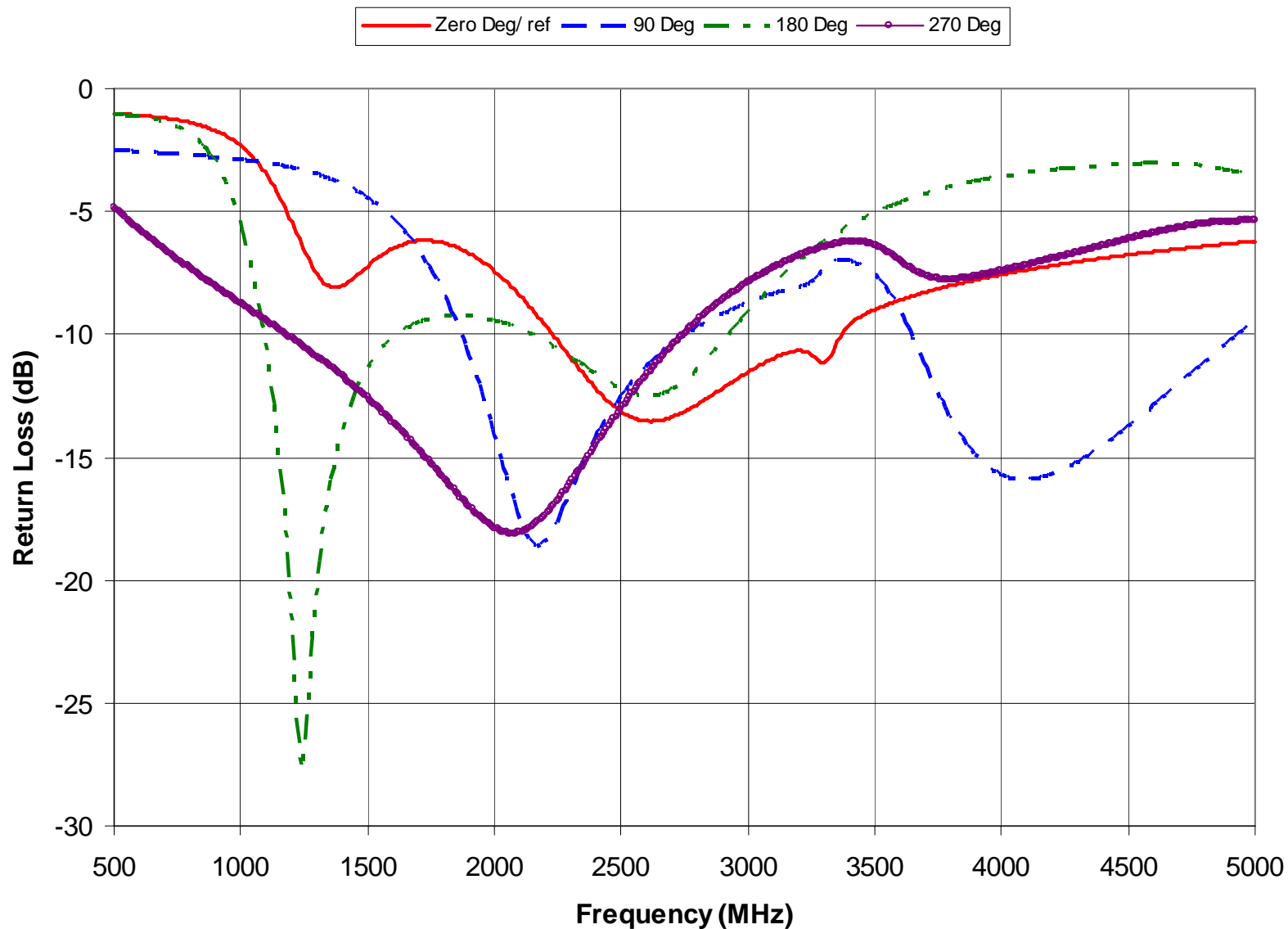
## Two Bit Phase Shifter Input Return Loss (S11)



## Two Bit Phase Shifter Output Return Loss (S22)

